

**DIGITAL LOGIC DESIGN**  
**SHARDA KUMARI**  
**BT20EC001**  
**ELECTRONICS AND COMMUNICATION**  
**EXPERIMENT 5**

## EXPERIMENT – 5

### AIM: -


Verification of the truth table of the Multiplexer 74150.

### APPARATUS REQUIRED: -

logic trainer kit, IC- 74150, wires.
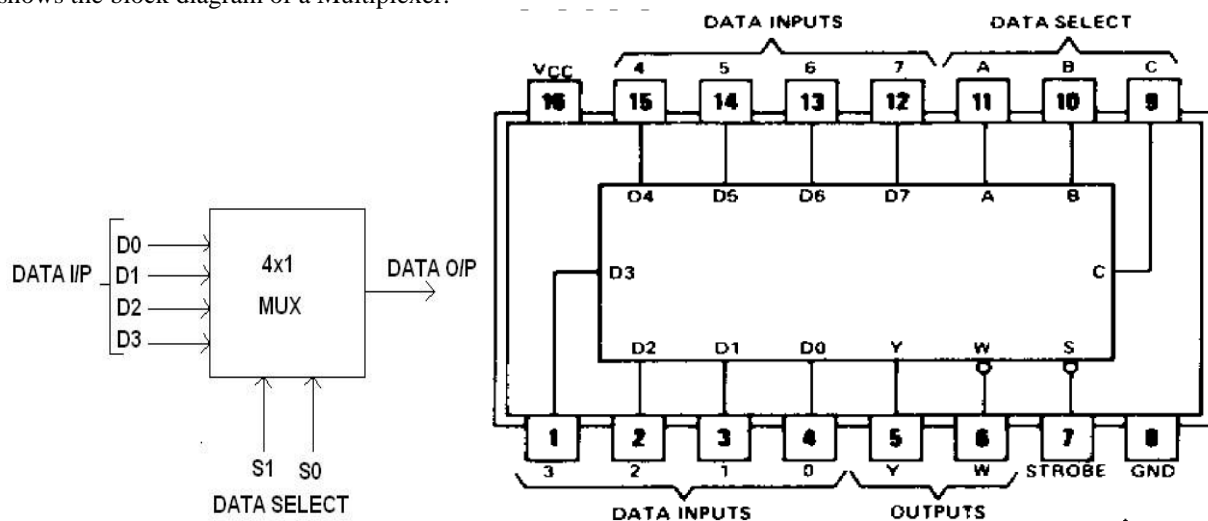
### THEORY:



A Multiplexer (or a data selector) is a logic circuit that accepts several data inputs and allows only one of them at a time to get through to the output. The selection of the desired data input is controlled by the SELECT (or ADDRESS) INPUTS. Multiplexer means transmitting a large number of information units over a smaller number of channels or lines. A digital multiplexer is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line. The selection of a particular input line is controlled by a set of selection lines. Normally there are  $2n$  input line and  $n$  selection lines whose bit combination determine which input is selected. Figure below shows the block diagram of a Multiplexer.



In this diagram the inputs and outputs are indicated by means of broad arrows to indicate that there may be one or more lines. Depending upon the digital code applied at the SELECT inputs, one out of the data sources is selected and transmitted to the single output channel. The Multiplexer becomes enabled when the strobe signal is active LOW. The pin out of a 8:1 multiplexer IC 74150 is shown above. The output of this circuit is the inverted input. This is a 16-pin DIP.

Function Table

INPUT		OUTPUT
S1	S0	Y
0	0	$D0 = D0 S1' S0'$
0	1	$D1 = D1 S1' S0$
1	0	$D2 = D2 S1 S0'$
1	1	$D3 = D3 S1 S0$
$Y = D0 S1' S0' + D1 S1' S0 + D2 S1 S0' + D3 S1 S0$		

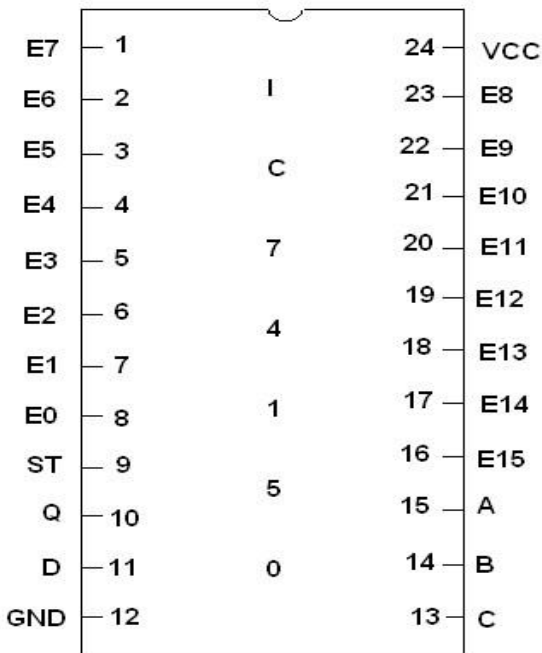
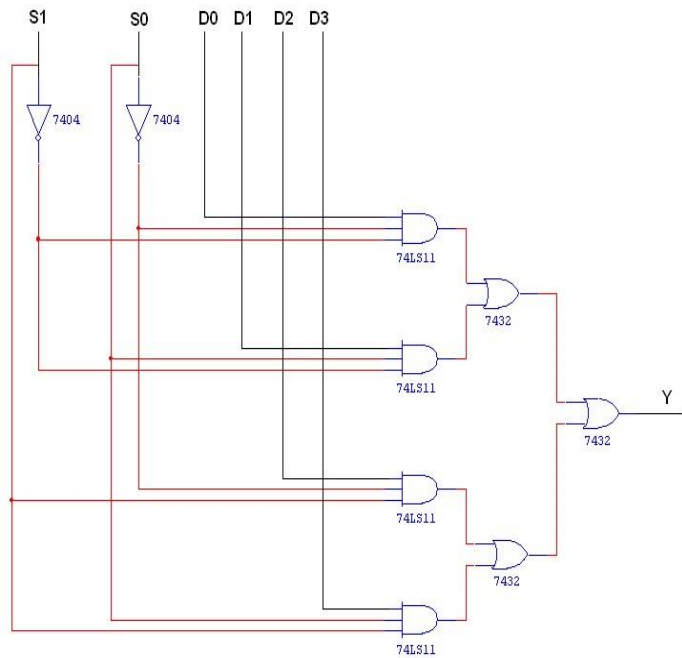
**PIN DIAGRAM:****CIRCUIT DIAGRAM FOR MULTIPLEXER:****Truth Table**


INPUT		OUTPUT
S1	S0	Y
0	0	D0
0	1	D1
1	0	D2
1	1	D3

**PROCEDURE: -**

- 1) Assemble the circuit on bread board, as per above diagram.
- 2) Give the logical inputs and check for the proper output, as per the truth table.

**VERIFICATION OF MULTIPLEXER:**

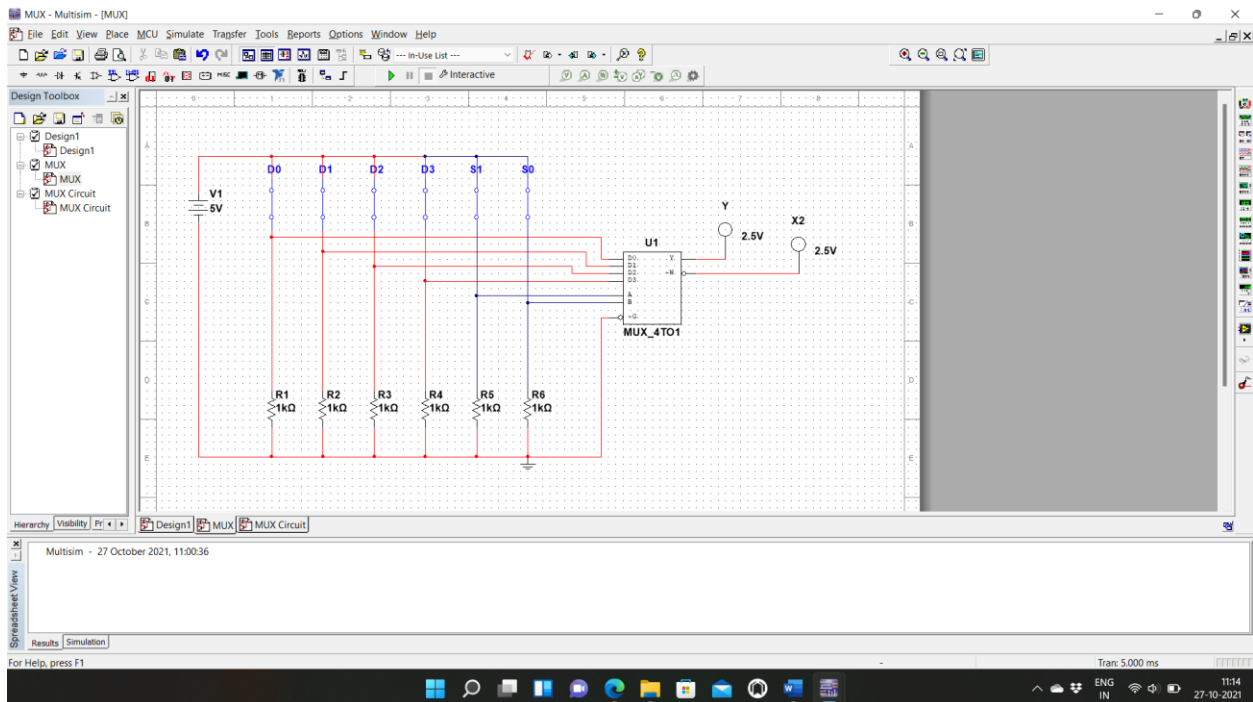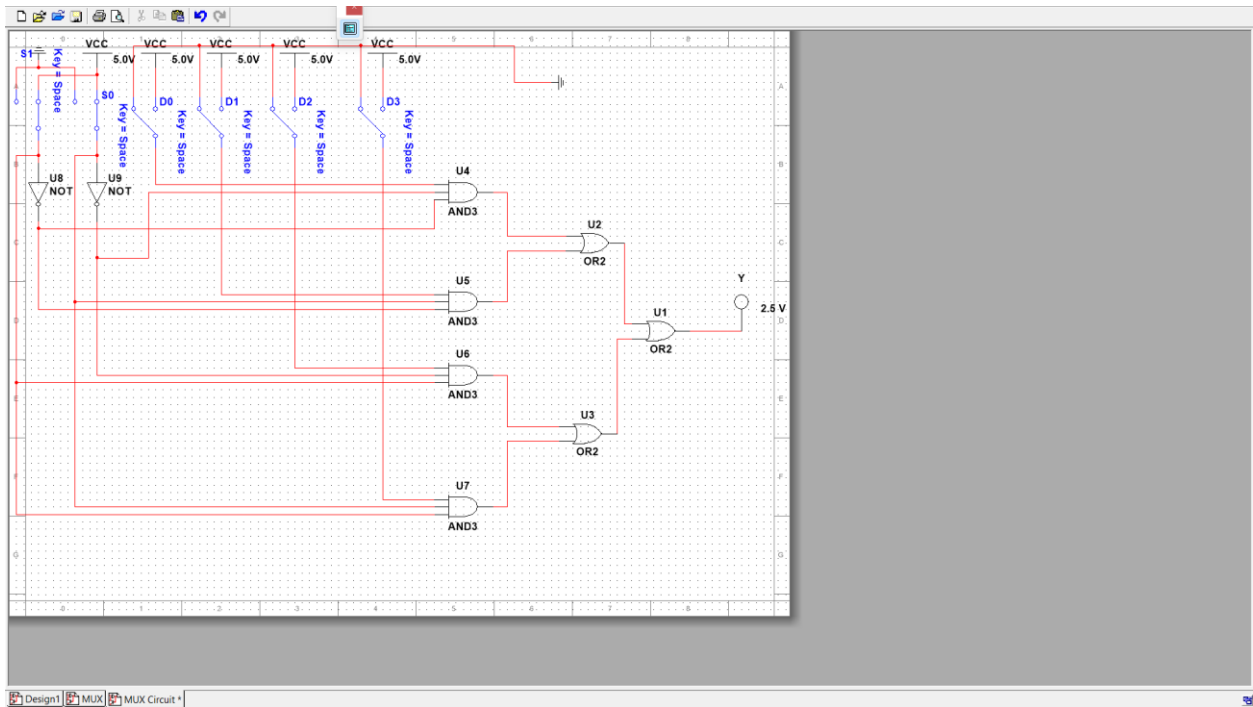

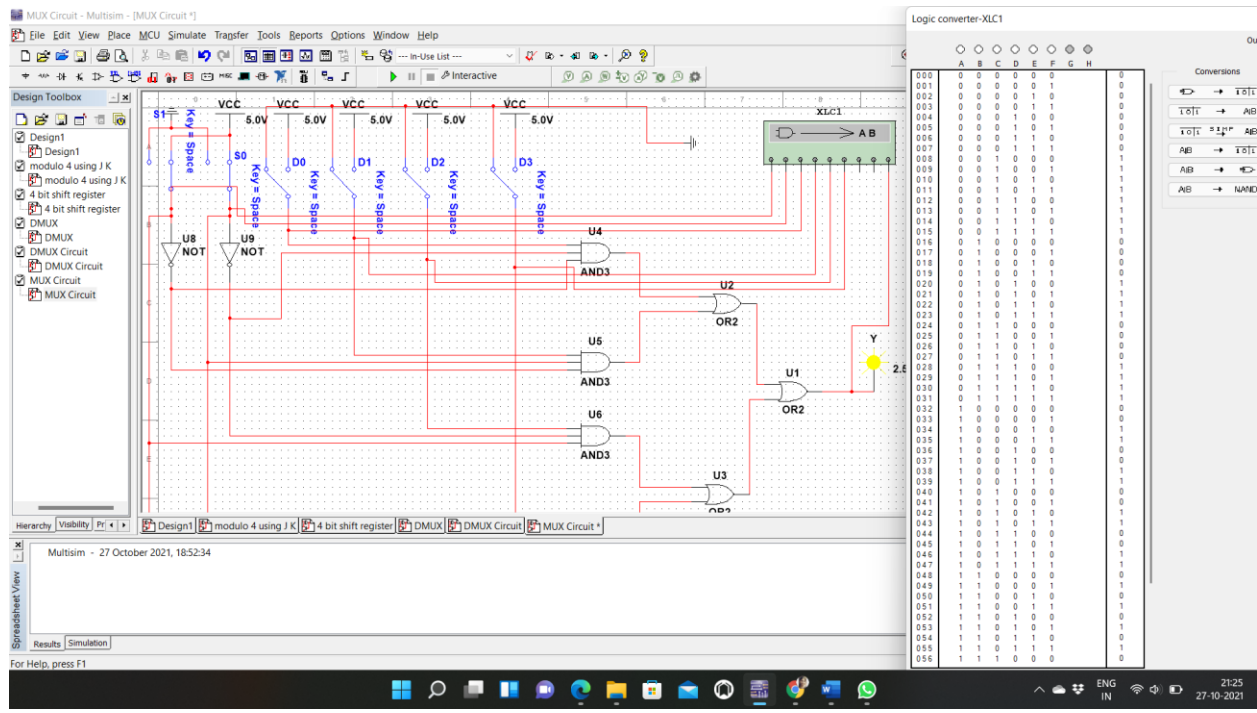

## CONCLUSION:

Hence verified the Multiplexer (8:1) operation using IC-74150

## PRECAUTIONS:

- All connections should be made neat and tight.
- Digital lab kits and ICs should be handled with utmost care.
- While making connections main voltage should be kept switched off.
- Never touch live and naked wires.