

**DIGITAL LOGIC DESIGN**  
**SHARDA KUMARI**  
**BT20EC001**  
**ELECTRONICS AND COMMUNICATION**  
**EXPERIMENT 10**

## EXPERIMENT – 10

### AIM: -

Operate the counters 7490, 7493.

### APPARATUS REQUIRED:-

Logic trainer kit, Counter ICs- 7490, IC - 7493 wires.


### THEORY:

#### **Asynchronous 74LS90 Decade Counter**

Digital counters count upwards from zero to some pre-determined count value on the application of a clock signal. Once the count value is reached, resetting them returns the counter back to zero to start again.

A decade counter counts in a sequence of ten and then returns back to zero after the count of nine. Obviously to count up to a binary value of nine, the counter must have at least four flip-flops within its chain to represent each decimal digit as shown.


#### **BCD Counter State Diagram**

 

#### **The 74LS90 BCD Counter**

The 74LS90 integrated circuit is basically a MOD-10 decade counter that produces a BCD output code. The 74LS90 consists of four master-slave JK flip-flops internally connected to provide a MOD-2 (count-to-2) counter and a MOD-5 (count-to-5) counter. The 74LS90 has one independent toggle JK flip-flop driven by the CLK A input and three toggle JK flip-flops that form an asynchronous counter driven by the CLK B input as shown.

#### **74LS90 BCD Counter**

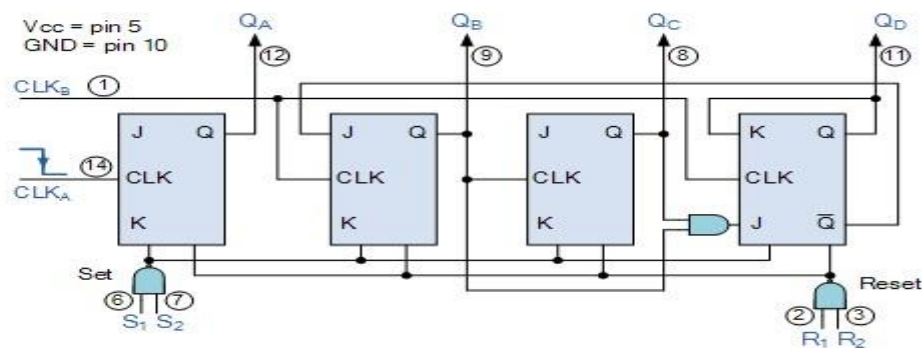

The counters four outputs are designated by the letter symbol Q with a numeric subscript equal to the binary weight of the corresponding bit in the BCD counter circuits code. So for example,  $Q_A$ ,  $Q_B$ ,  $Q_C$  and  $Q_D$ . The 74LS90 counting sequence is triggered on the negative going edge of the clock signal, that is when the clock signal CLK goes from logic 1 (HIGH) to logic 0 (LOW).


The additional input pins  $R_1$  and  $R_2$  are counter “reset” pins while inputs  $S_1$  and  $S_2$  are “set” pins. When connected to logic 1, the Reset inputs  $R_1$  and  $R_2$  reset the counter back to zero, 0 (0000), and when the Set inputs  $S_1$  and  $S_2$  are connected to logic 1, they Set the counter to maximum, or 9 (1001) regardless of the actual count number or position.

## **PROCEDURE:**

- (i) Connections are given as per circuit diagram.
- (ii) Logical inputs are given as per circuit diagram.
- (iii) Observe the output and verify the truth table.

## **CIRCUIT DESIGN:**

### **ASYNCHRONOUS DECADE COUNTER**

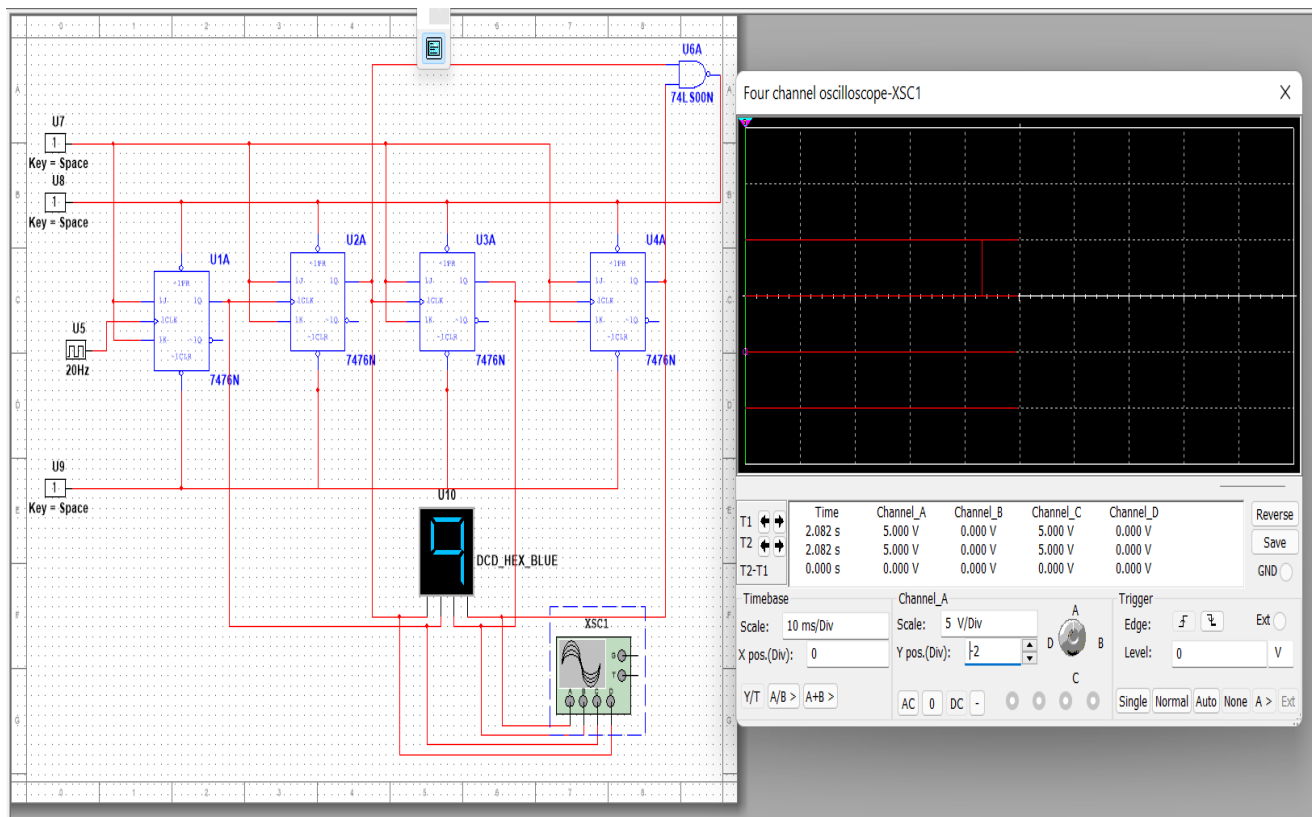

The screenshot displays the Multisim software environment with a digital logic circuit simulation. The circuit is a 4-bit counter implemented using four JK flip-flops (U1, U2, U3, U4) cascaded together. A 100Hz clock source (U9) provides a common clock signal to all flip-flops. The output of the first flip-flop (U1) is connected to the clock of the second (U2), and so on. The output of the fourth flip-flop (U4) is connected to a 2.5V LED indicator (X4). The circuit is powered by a 5.0V VCC source. The Design Toolbox on the left shows the components used: bcd counter, mod 10 counter, and JK\_FF.

Thus the Counters were designed and their truth table is verified.

- All connections should be made neat and tight.
- Digital lab kits and ICs should be handled with utmost care.
- While making connections main voltage should be kept switched off.
- Never touch live and naked wires.