

DIGITAL LOGIC DESIGN
SHARDA KUMARI
BT20EC001
ELECTRONICS AND COMMUNICATION
EXPERIMENT 6

EXPERIMENT – 6

AIM: -

Verification of the truth table of the De-Multiplexer 74154.

APPARATUS REQUIRED: -



Logic trainer kit, IC- 74154, wires.

THEORY:

A Demultiplexer performs the reverse operation of a Multiplexer. It accepts a single input and distributes it over several outputs. The SELECT input code determines to which output the data input will be transmitted. The Demultiplexer becomes enabled when the strobe signal is active LOW.

This circuit can also be used as binary-to-decimal decoder with binary inputs applied at the select input lines and the output will be obtained on the corresponding line. These devices are available as 2-line-to-4-line decoder, 3-line-to-8-line decoder, 4-line-to-16-line decoder. The output of these devices is active LOW. Also there is an active low enable/data input terminal available. Figure below shows the block diagram of a Demultiplexer.

BLOCK DIAGRAM FOR 1:4 DEMULTIPLEXER:

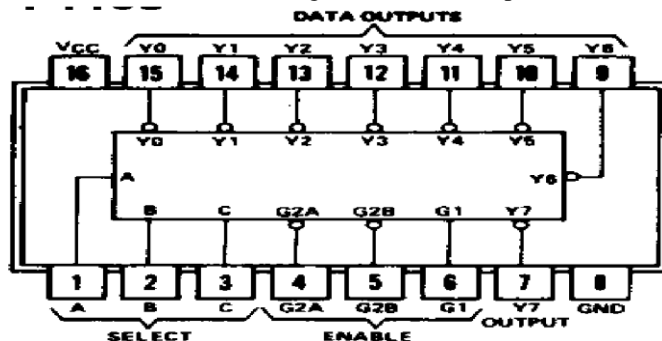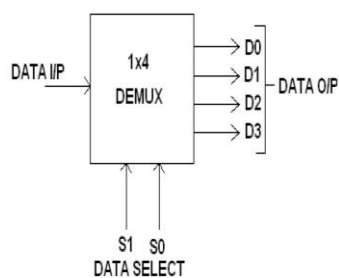


PIN CONFIGURATION:

FUNCTION TABLE:		
S1	S0	INPUT
0	0	$D0 = X S1' S0$
0	1	$D1 = X S1' S0'$
1	0	$D2 = X S1 S0'$
1	1	$D3 = X S1 S0$
$Y = X S1' S0 + X S1' S0' + X S1 S0' + X S1 S0$		

In this diagram the inputs and outputs are indicated by means of broad arrows to indicate that there may be one or more lines. Depending upon the digital code applied at the SELECT inputs, one data is transmitted to the single output channel out of many. The pin out of a 16:1 Demultiplexer IC 74154 is shown above. The output of this circuit is active low. This is a 24-pin DIP.

CIRCUIT DIAGRAM:

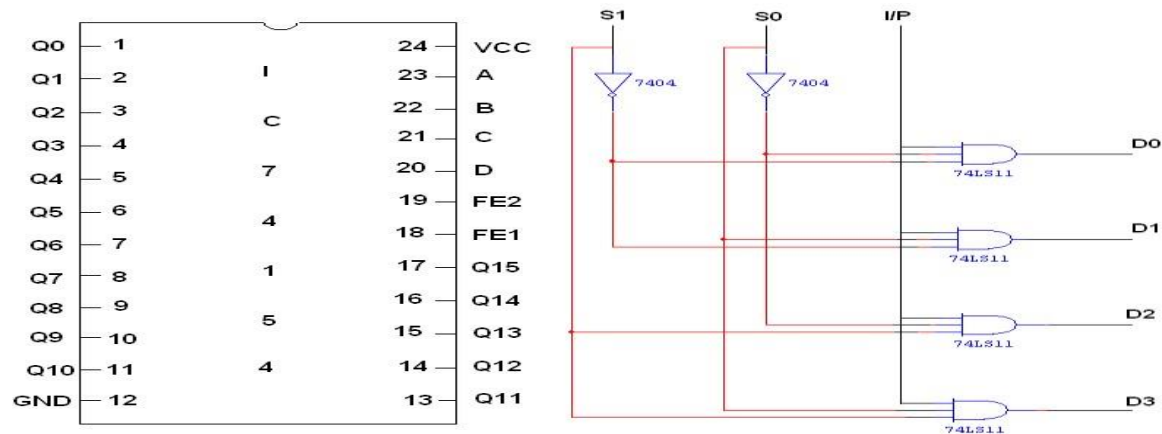



PIN DIAGRAM:


TRUTH TABLE						
INPUT			OUTPUT			
S1	S0	I/P	D0	D1	D2	D3
0	0	0	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	0	0
1	0	1	0	0	1	0
1	1	0	0	0	0	0
1	1	1	0	0	0	1


PROCEDURE: -

- 1) Assemble the circuit on bread board, as per above Pin diagram.
- 2) Give the logical inputs and check for the proper output, as per the truth table.

VERIFICATION OF DEMULTIPLEXER:

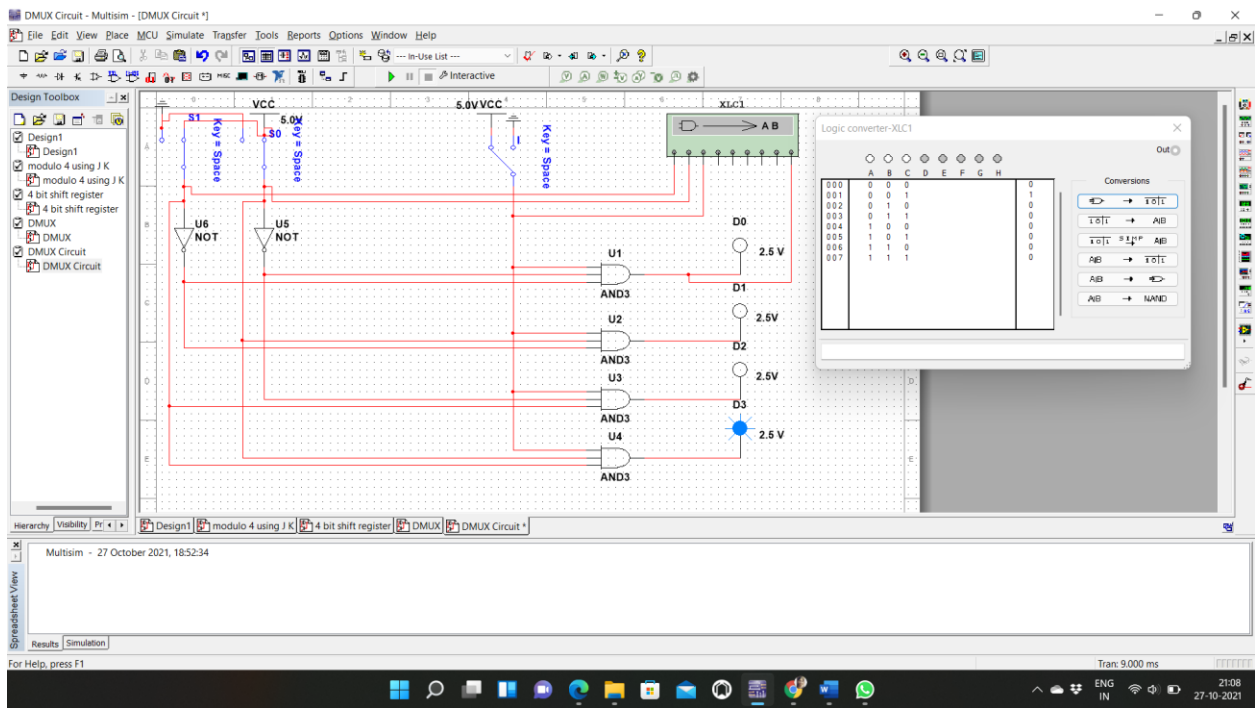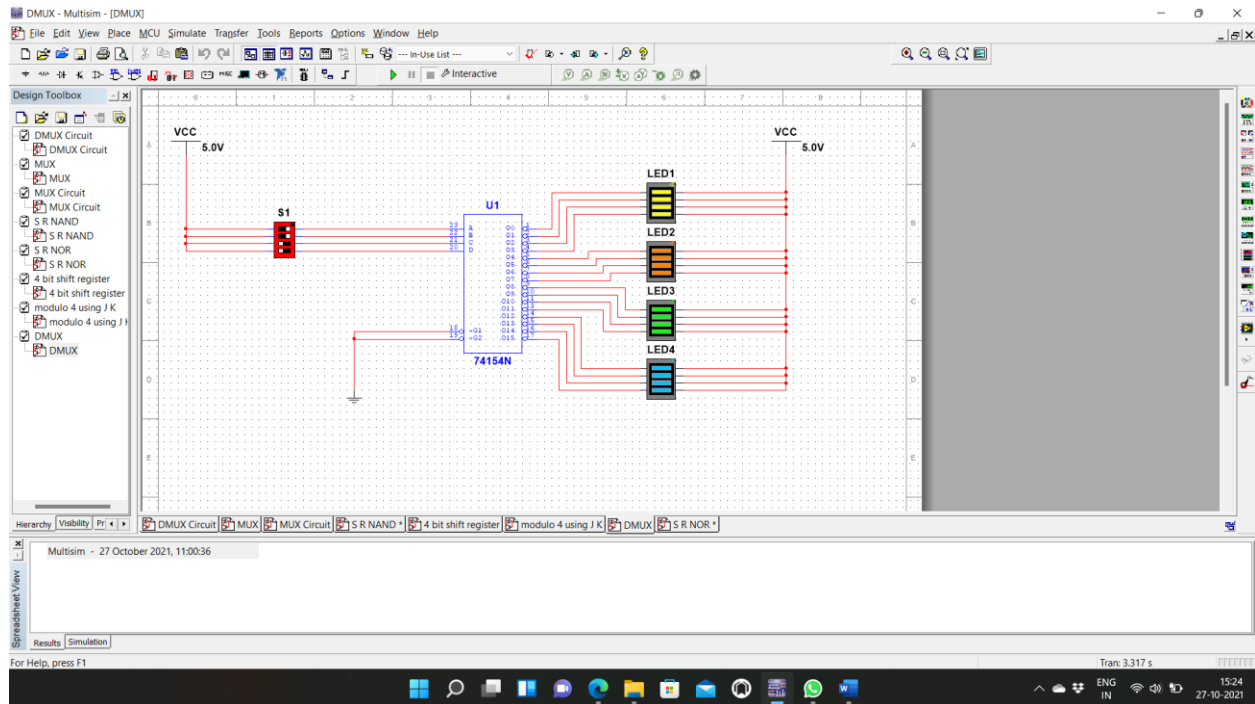

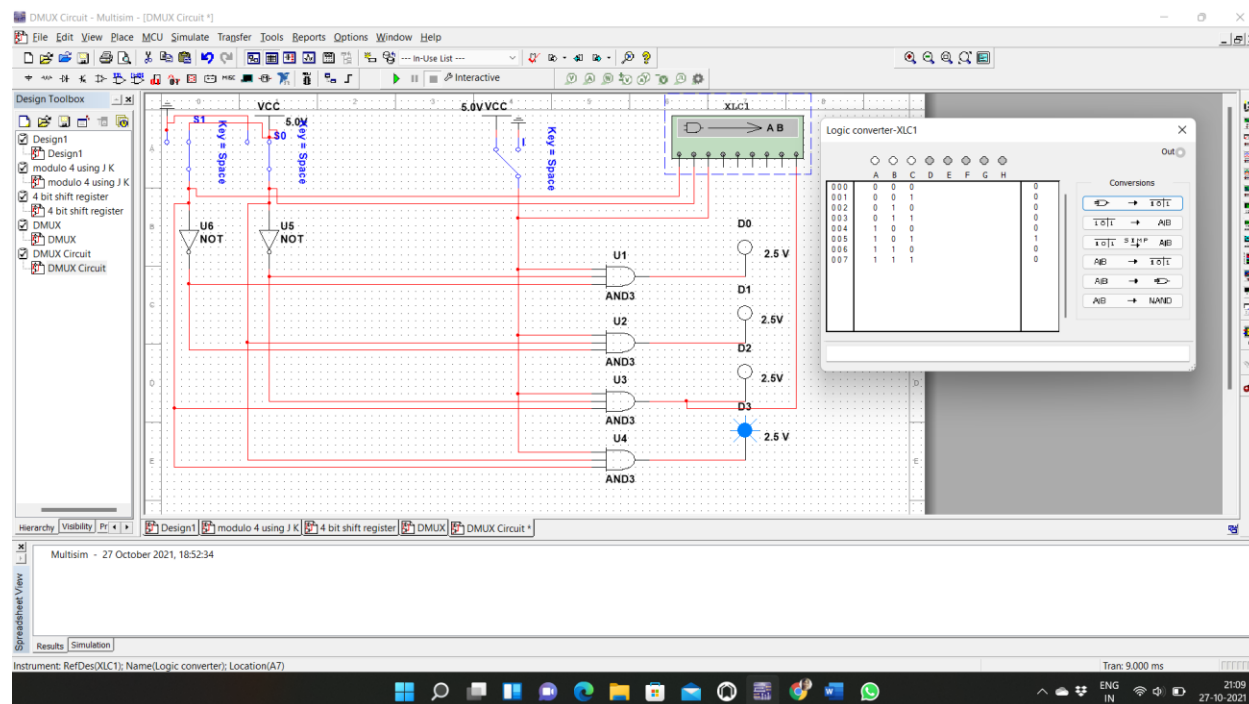

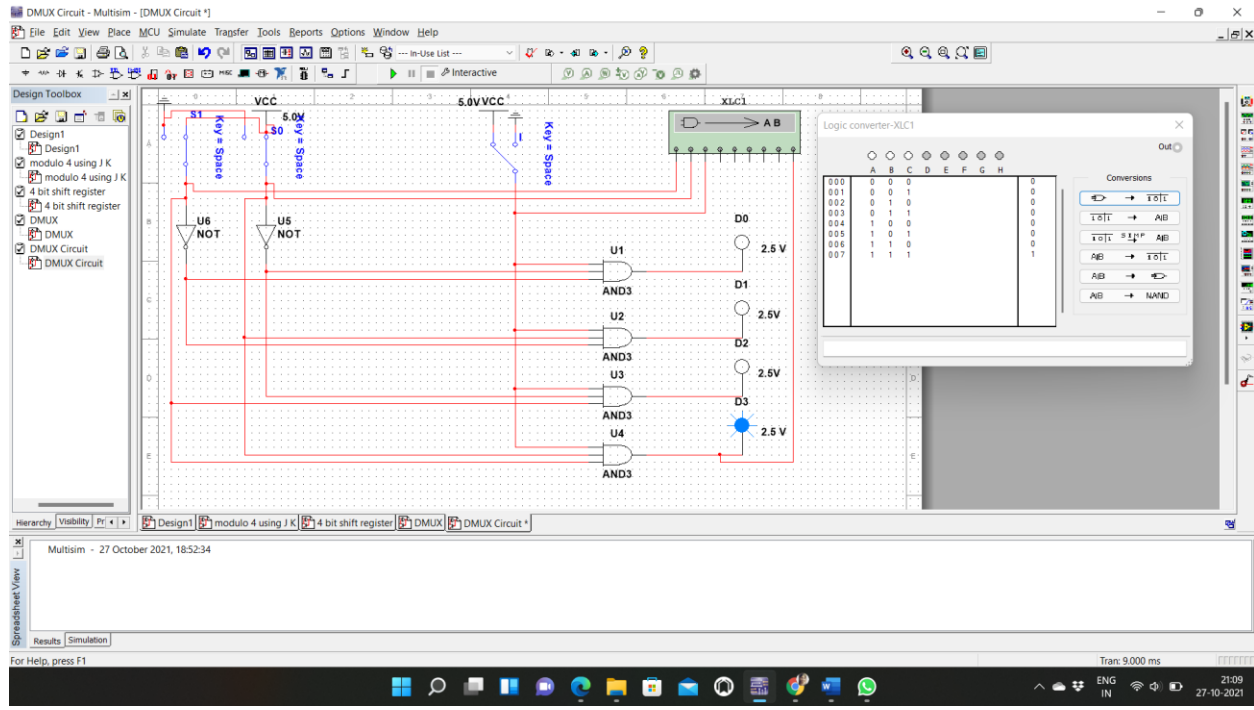

CONCLUSION:

Hence verified the Demultiplexer (16:1) operation using IC-74154.

PRECAUTIONS:

- All connections should be made neat and tight.
- Digital lab kits and ICs should be handled with utmost care.
- While making connections main voltage should be kept switched off.
- Never touch live and naked wires.