

DIGITAL LOGIC DESIGN

SHARDA KUMARI

BT20EC001

ELECTRONICS AND COMMUNICATION

EXPERIMENT 3

EXPERIMENT – 3

AIM: -

Design and verification of the truth tables of Half and Full adder circuits.

APPARATUS REQUIRED: -

logic trainer kit, NAND gates (IC 7400), XOR gates (IC 7486), AND gates (IC 7408), wires.

THEORY:

half adder:

A half adder has two inputs for the two bits to be added and two outputs one from the sum 'S' and other from the carry 'C' into the higher adder position. Above circuit is called as a carry signal from the addition of the less significant bits sum from the X-OR Gate the carry out from the AND gate.

Truth Table for Half Adder

INPUT		OUTPUT	
A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

K-Map for SUM:


B	00	01
A 00		1
A 01	1	

$$\text{SUM} = A'B + AB'$$

K-Map for CARRY: Half Adder using basic gates:-

B	00	01
A 00		
A 01		1

$$\text{CARRY} = AB$$

 


$$S = \bar{A}B + A\bar{B}$$

$$S = A \oplus B$$

$$C = AB$$

Half Adder using NAND gates only:-

 


Full Adder:

A full adder is a combinational circuit that forms the arithmetic sum of input; it consists of three inputs and two outputs. A full adder is useful to add three bits at a time but a half adder cannot do so. In full adder sum output will be taken from X-OR Gate, carry output will be taken from OR Gate.

Truth Table for Full Adder

K-Map for SUM:



K-Map for CARRY:

 

$$\text{CARRY} = AB + BC + AC$$

7486


A

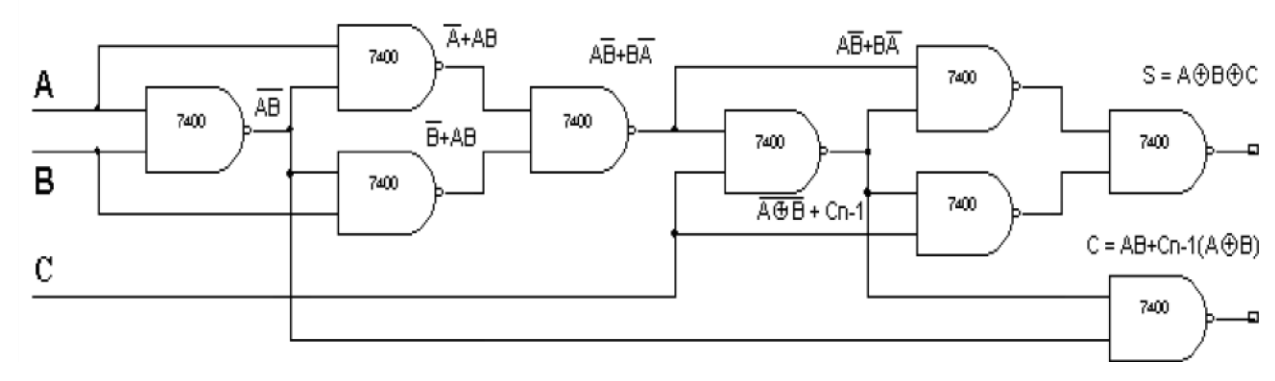 


VERIFICATION OF HALF ADDER:

HALF ADDER USING BASIC GATES:

SUM

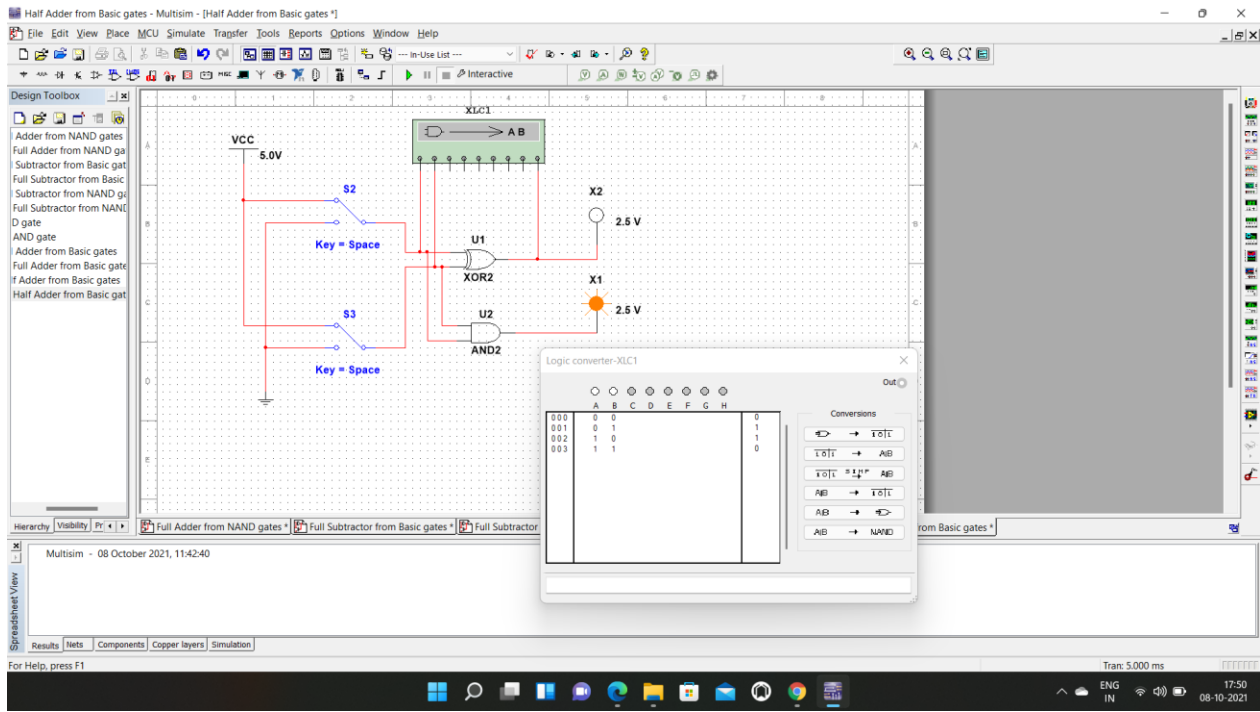


CARRY

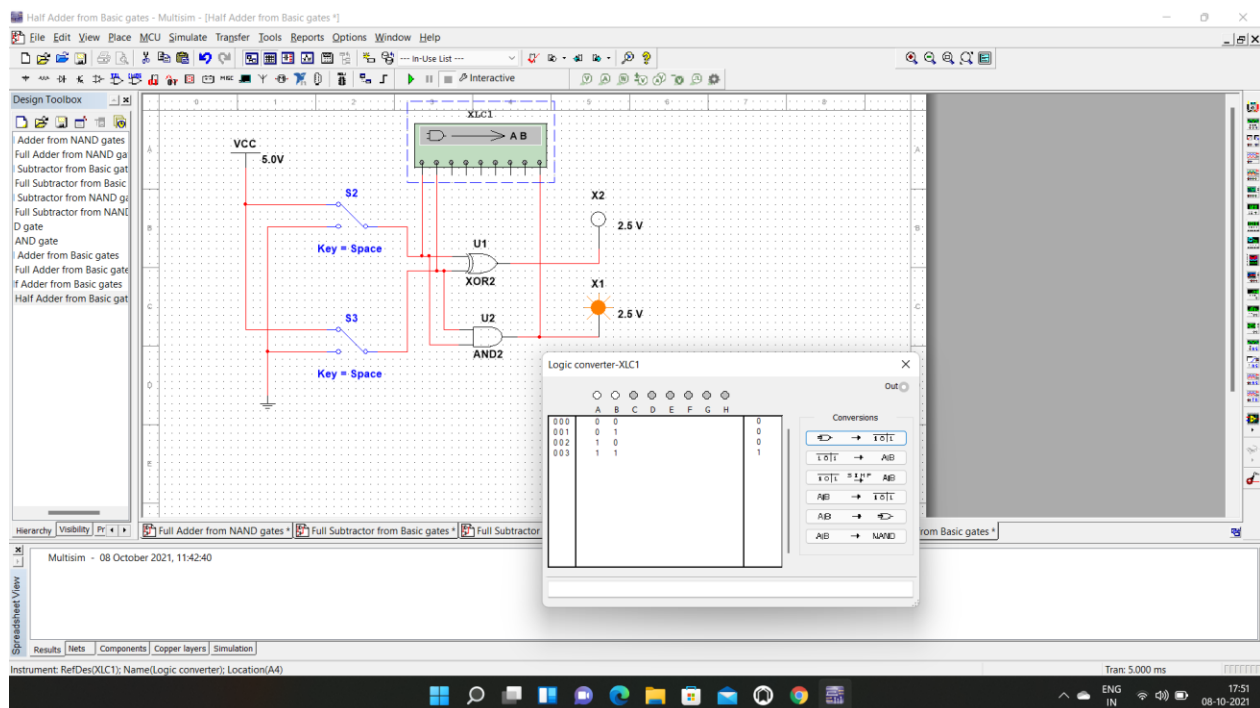


HALF ADDER USING NAND GATES:

SUM

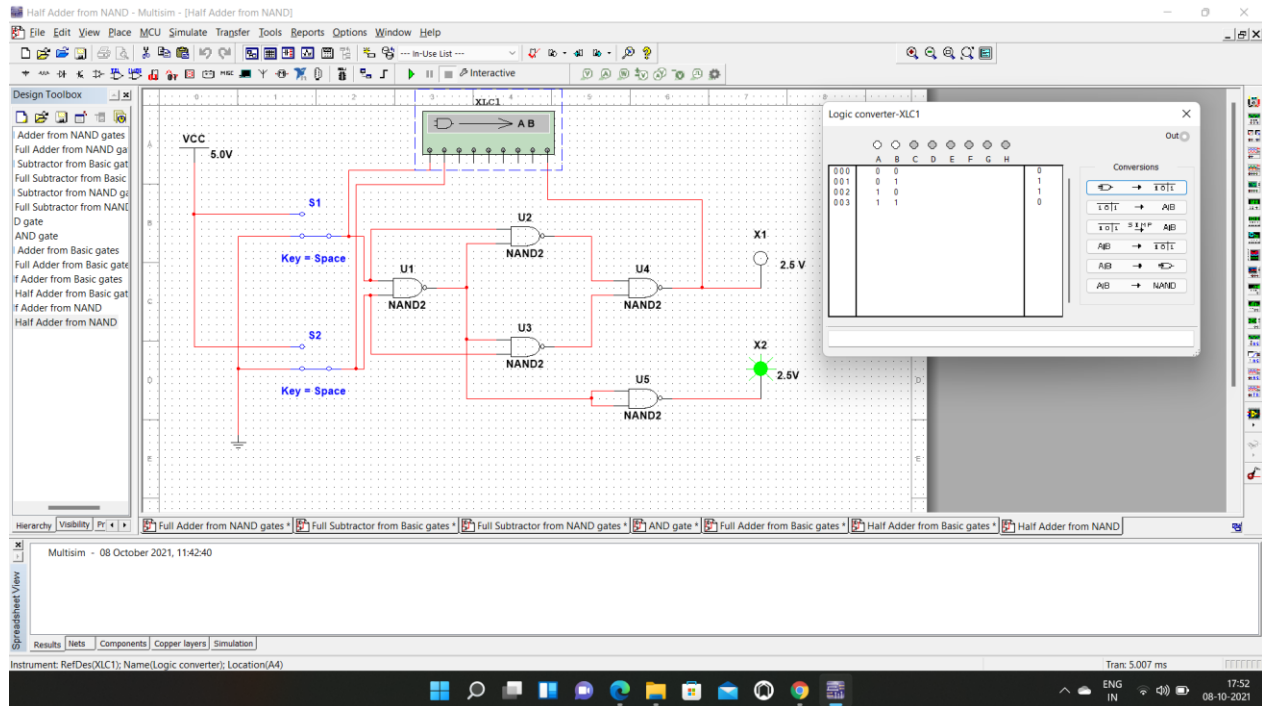


CARRY

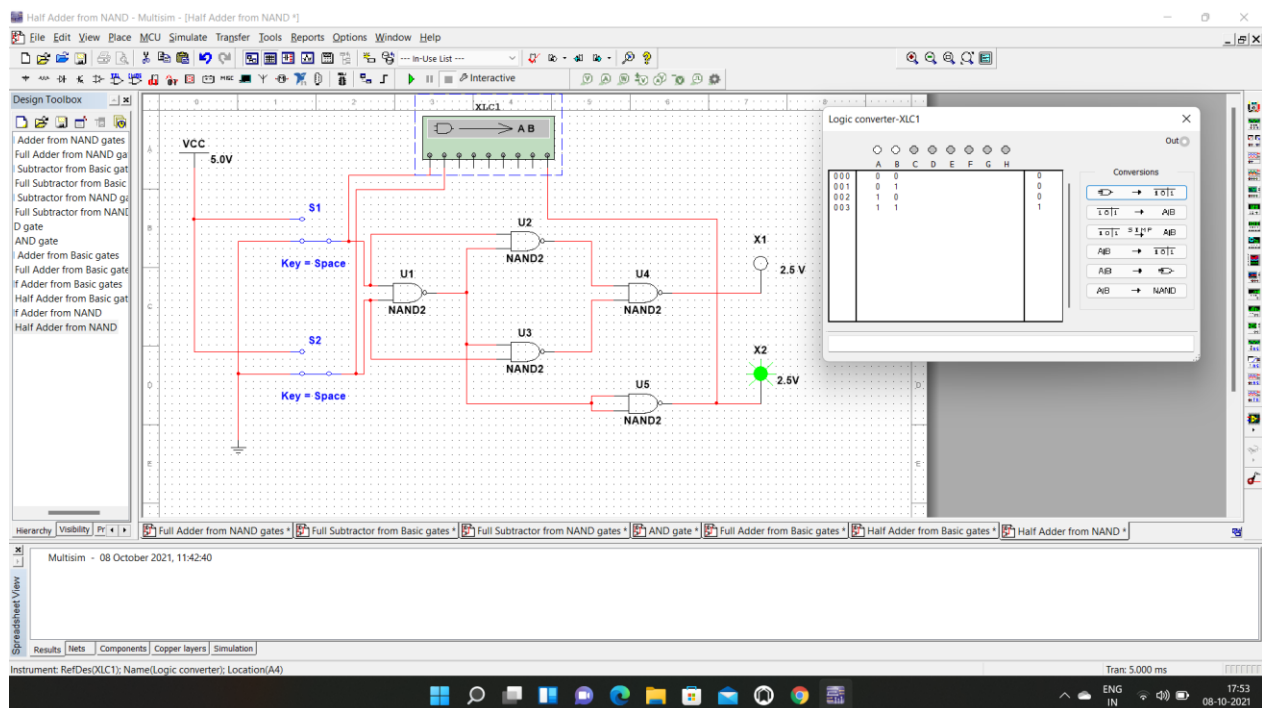


VERIFICATION OF FULL ADDER:

FULL ADDER USING BASIC GATES:

SUM

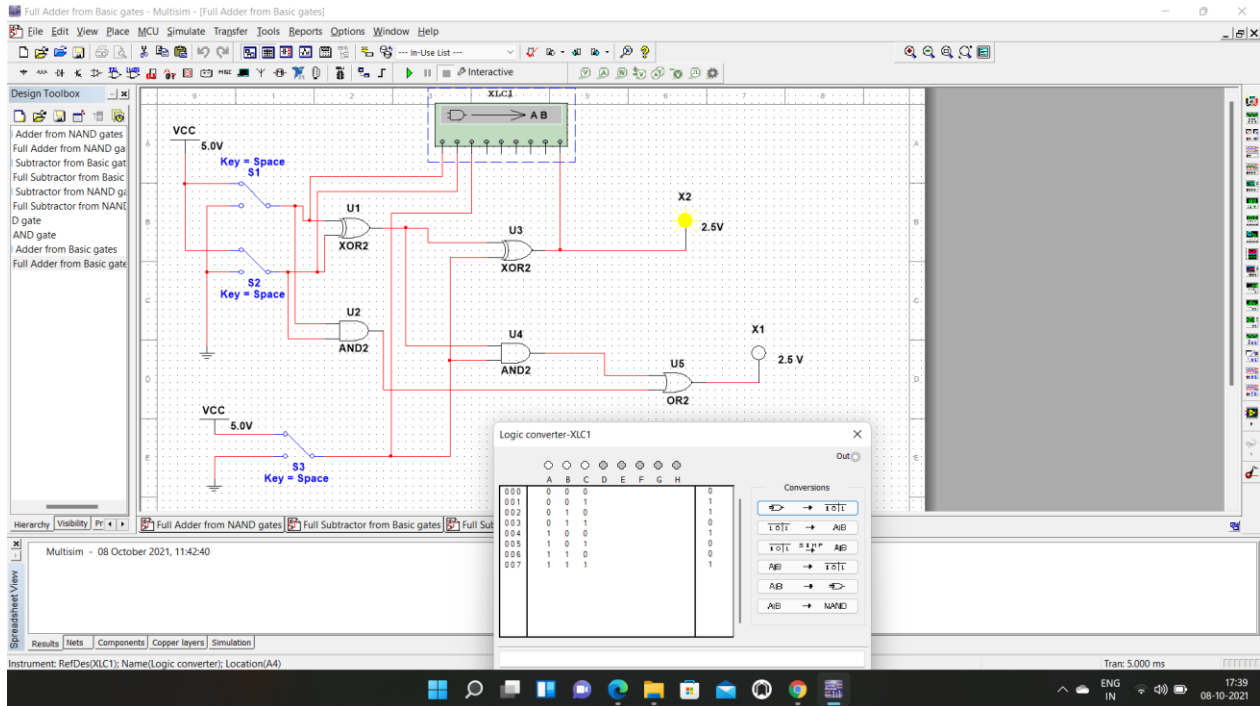


CARRY

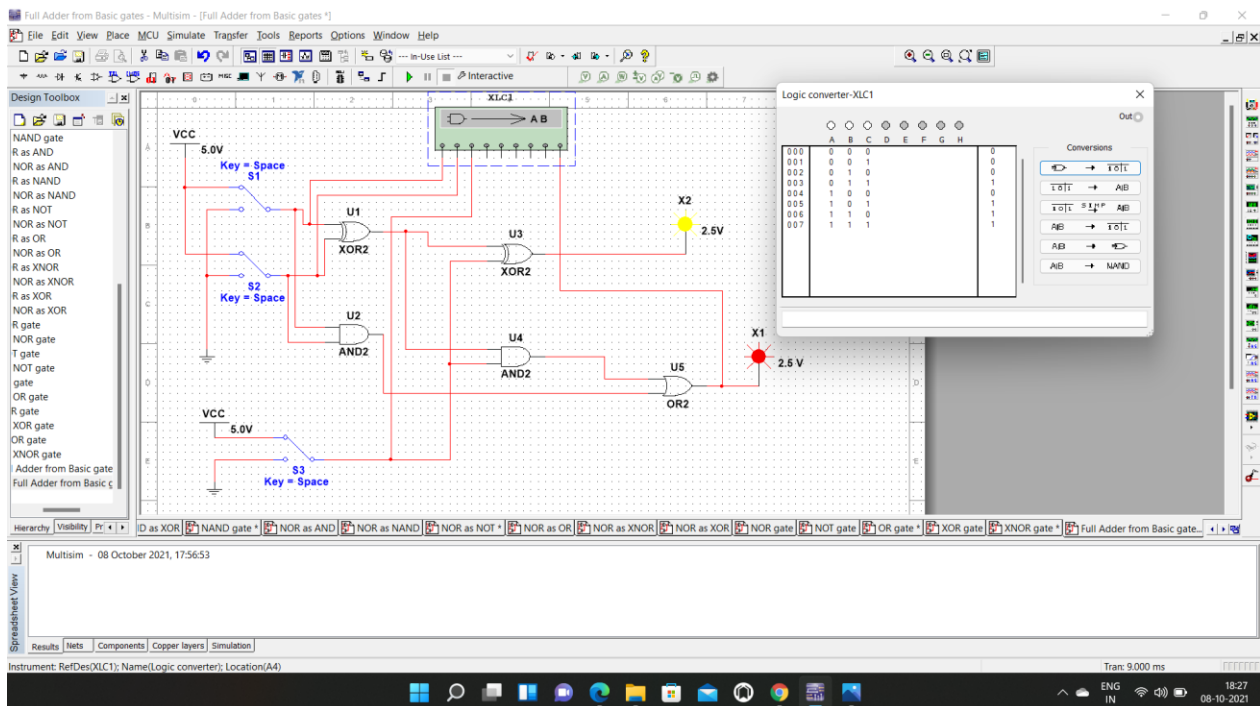


FULL ADDER USING NAND GATES:

SUM

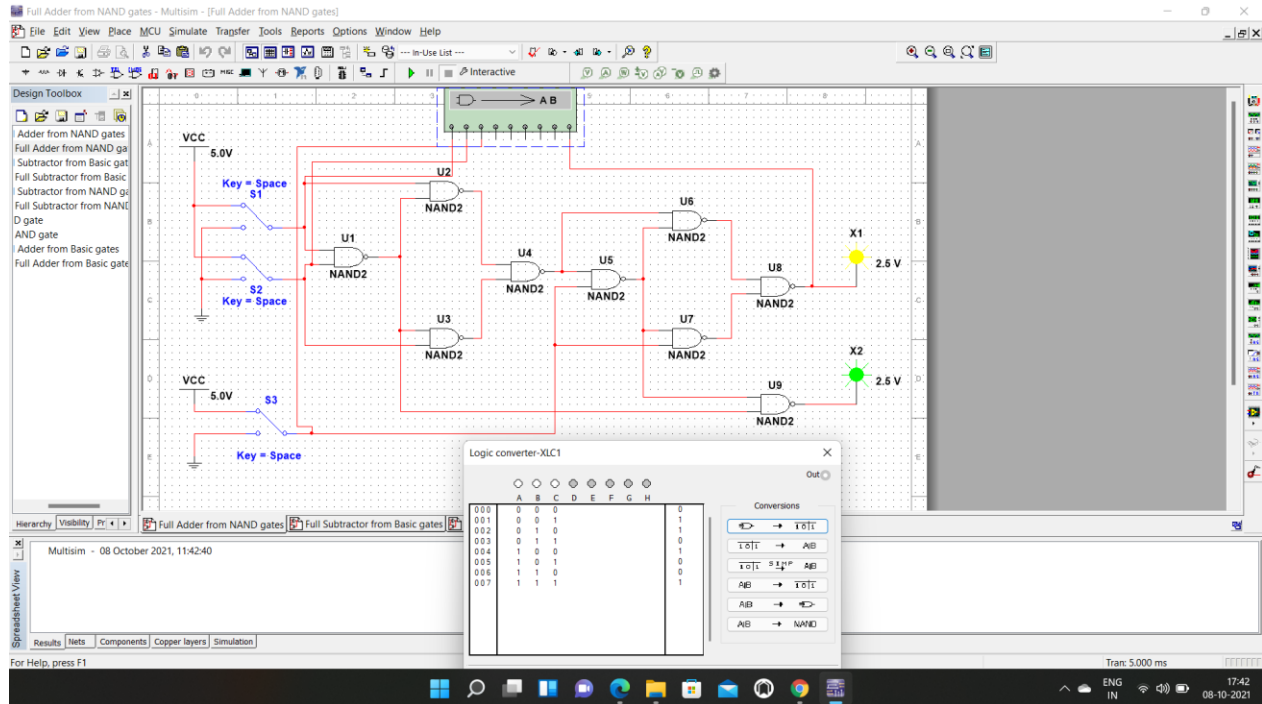

CARRY

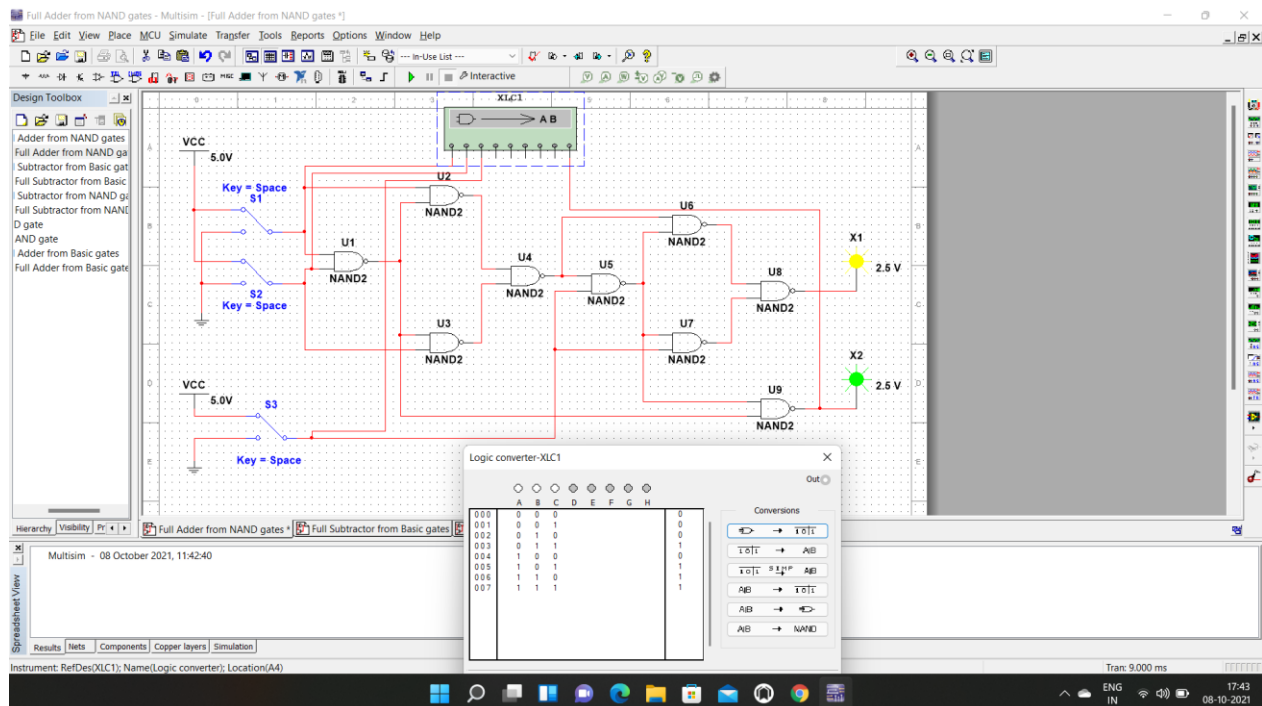

PROCEDURE:

- (i) Connections are given as per circuit diagram.
- (ii) Logical inputs are given as per circuit diagram.
- (iii) Observe the output and verify the truth table.

RESULT:

Thus the half adder & full adder was designed and their truth table is verified.

PRECAUTIONS:

- All connections should be made neat and tight.
- Digital lab kits and ICs should be handled with utmost care.
- While making connections main voltage should be kept switched off. • Never touch live and naked wires.